

# Why do tube amplifiers have fat sound while solid state amplifiers don't

Shengchao Li

Oct 21, 2011

# Summary


- ▶ Tube amplifiers have:
  - ▶ “**Fat sound**”: “warm”, “clean”, “soft”, “smooth”, “fat”, “detailed”, “euphonic” ...
  - ▶ “**Vivid sound**”: “euphonic”, “life like”, “vivid” ...
- ▶ I show **tube amplifiers are speaker cone excursion soft limiters**, due to output transformer core nonlinearity
- ▶ High frequency signal is not affected by transformer nonlinearity, even when superposed with low frequency signal with excessive amplitude
- ▶ I think it can explain “fat sound”
- ▶ It calls for validation from listening tests

# How the Poster is Organized


- ▶ Part 1. Simulations show tube amplifiers are speaker cone excursion soft limiters
- ▶ Part 2. Block diagram manipulation relates tube amplifiers to existing soft speaker cone excursion limiters
- ▶ Part 3. Experiments

Part 1, Simulations show tube amplifiers are speaker cone excursion soft limiters

# A typical SET amplifier

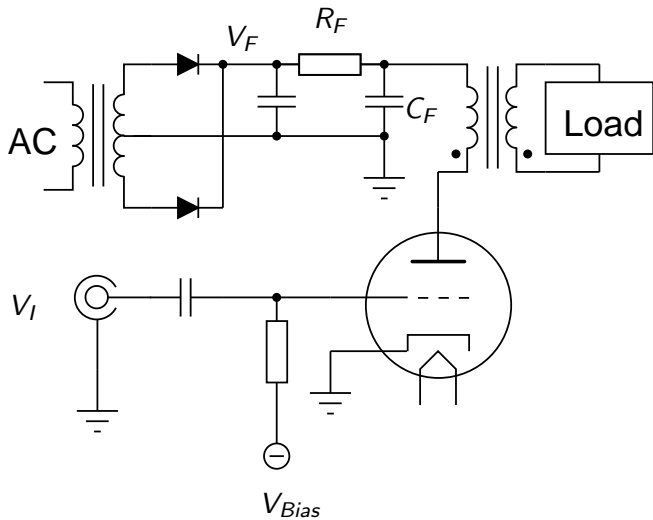
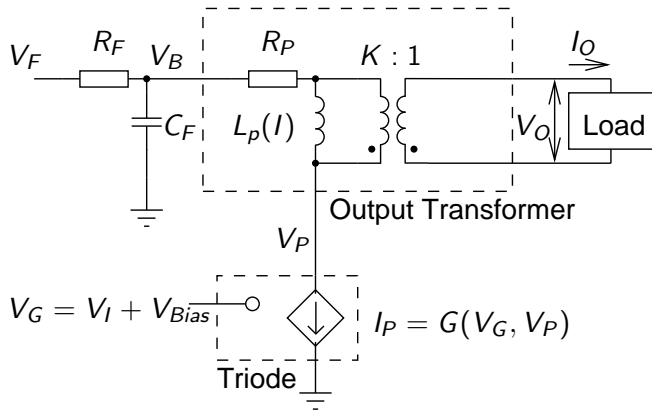
# Equivalent Circuit of the Typical SET Amplifier



## Equations describing the Equivalent Circuit


$$V_B = \frac{1}{C_F} \int^t \left( \frac{V_F - V_B}{R_F} - I_P \right) d\tau$$

$$I_P = G(V_I + V_{Bias}, V_B - KV_O - I_P R_P)$$


$$V_O = \frac{N}{K} \frac{d}{dt}(-\Phi) = \frac{NA}{K} \frac{d}{dt} B \left( \frac{N}{l} \left( I_P - \frac{I_O}{K} \right) \right)$$

- ▶  $B(\cdot)$  is core  $B(H)$  function
- ▶  $A$  is the area of the core
- ▶  $N$  is number of turns of primary winding
- ▶  $l$  is the length of the magnetic path
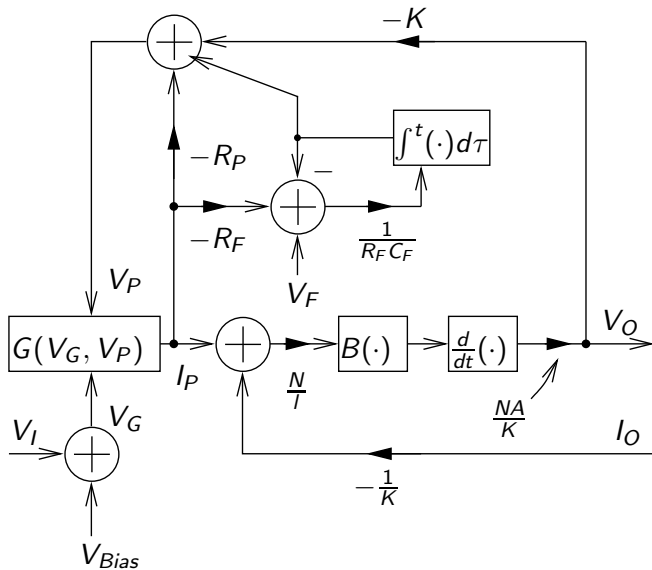
# Equivalent Block Diagram Derived from the Equations



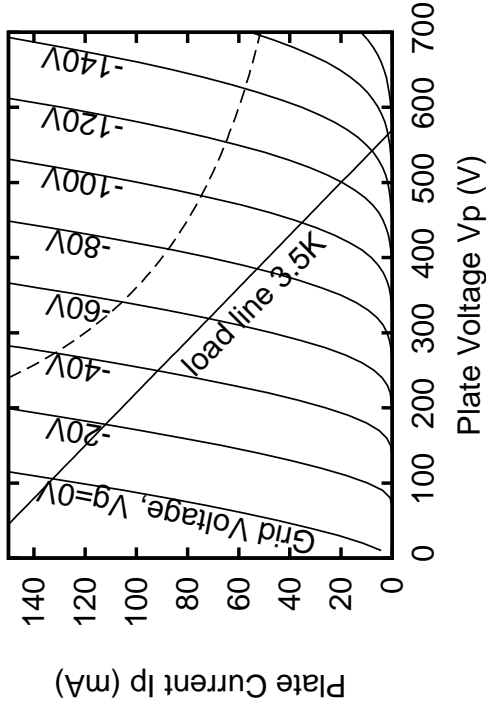
The Function  $I_P = G(V_G, V_P)$  of 300B Tube



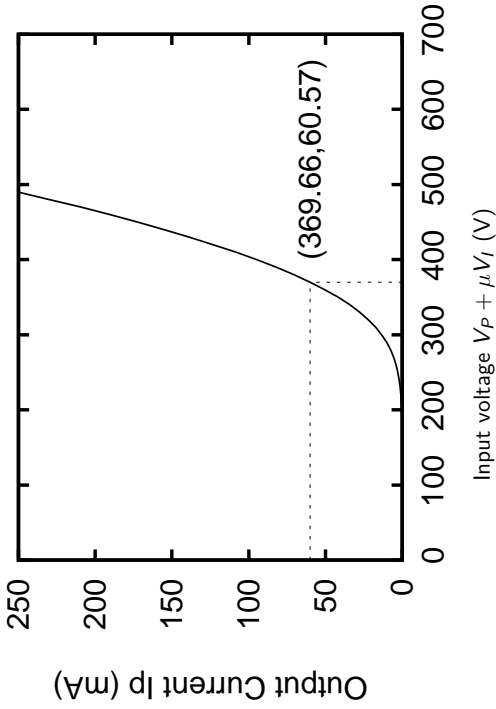
## Function $I_P = G(V_G, V_P)$ Can Be Simplified

- ▶ The curves with different  $V_G$ 's are approximately parallel
- ▶ It is unlikely that the triode will operate near bottom left corner
- ▶ Thus the curve can be simplified (depicted in next Figure).
- ▶ An operation point (369.66, 60.57) is shown.


$I_P = G(V_G, V_P)$  Simplified to  $G(V_P + \mu V_I)$



# Equivalent Block Diagram Simplified

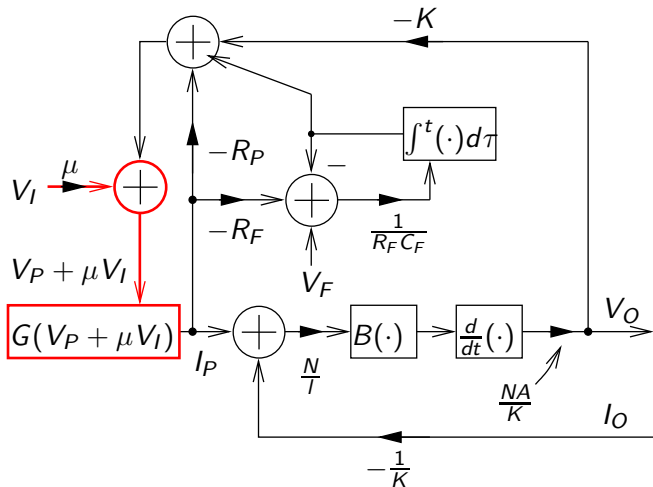

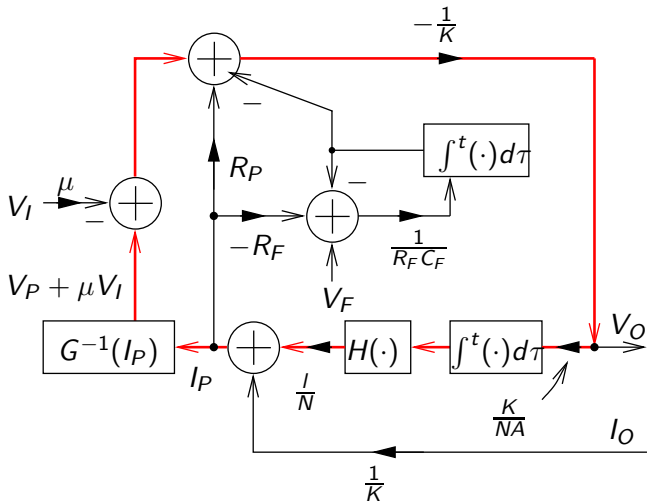
# Equivalent Block Diagram w/ a Big Loop Reversed




Refer to Shengchao li, "Loop Reversal Technique in Block Diagram or Signal Flow Graph Manipulation", unpublished technical report, 2011

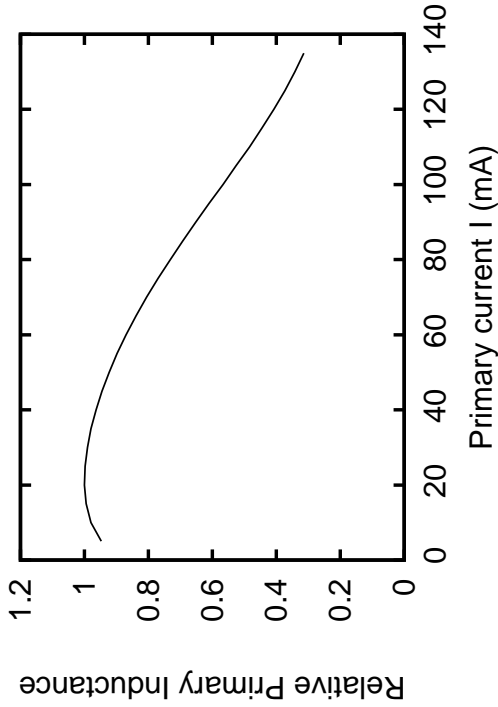
# Measured relative inductance of transformer A



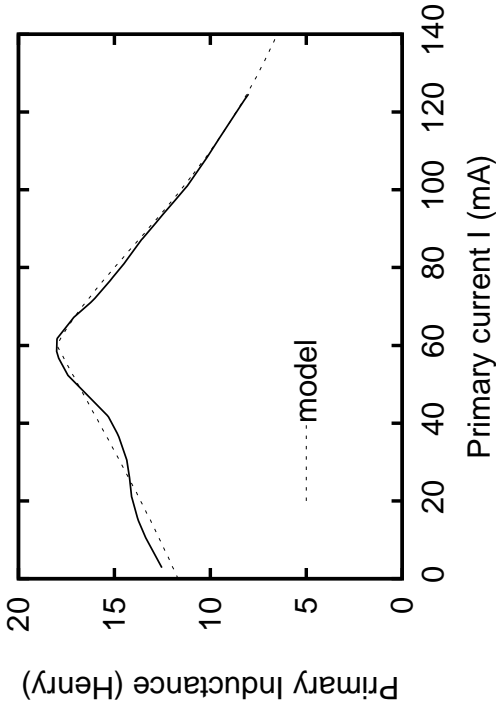
# Measured relative inductance of transformer B



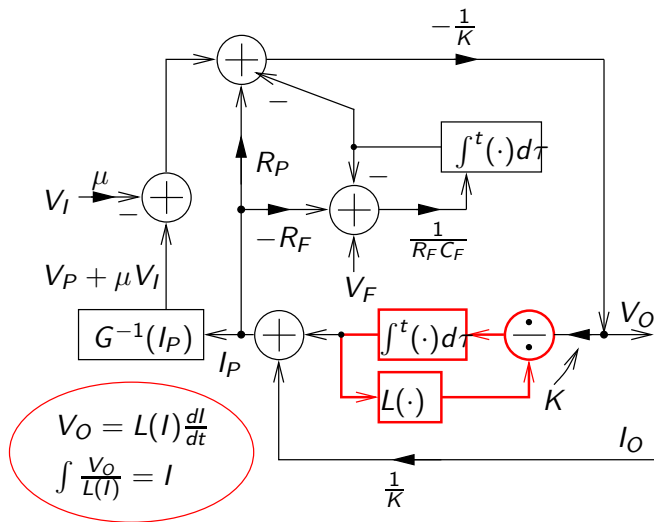
# Can Simulate with the Inductance Curve Directly



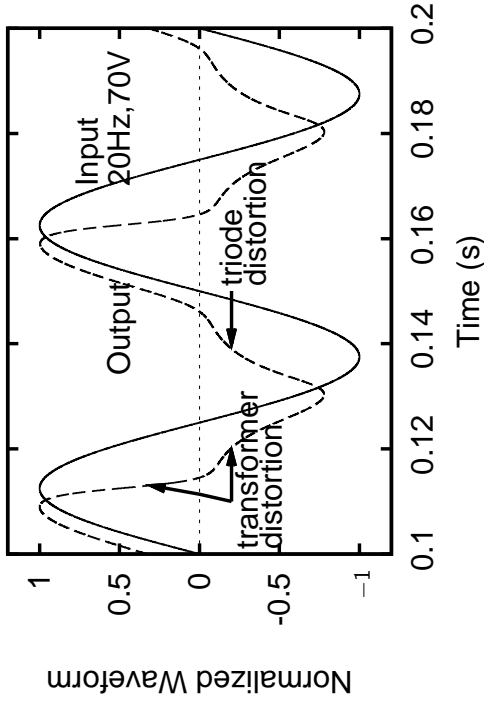
$V_O$  v.s.  $V_I$  with low frequency input signal with excessive amplitude: Speaker Cone Excursion Softly Limited



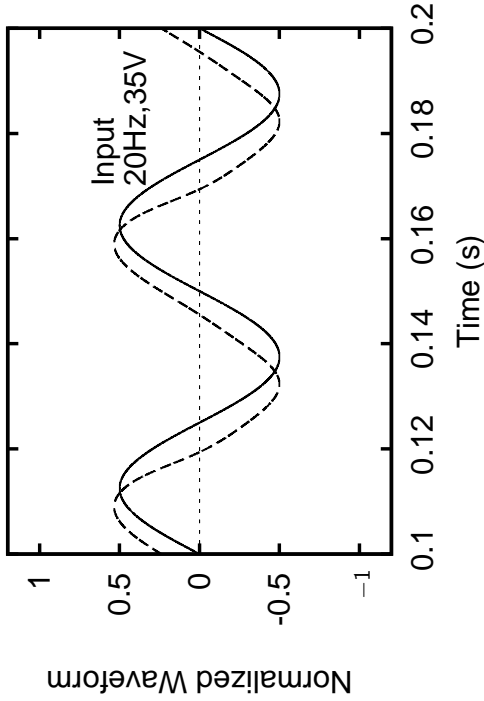
$V_O$  v.s.  $V_I$  with low frequency input signal with moderate amplitude: No or little soft limiting



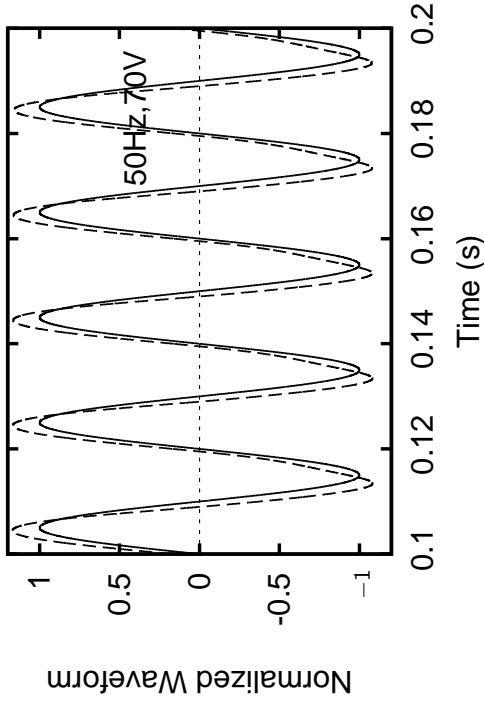
$V_O$  v.s.  $V_I$  with moderately high frequency input signal with high amplitude: No or little soft limiting



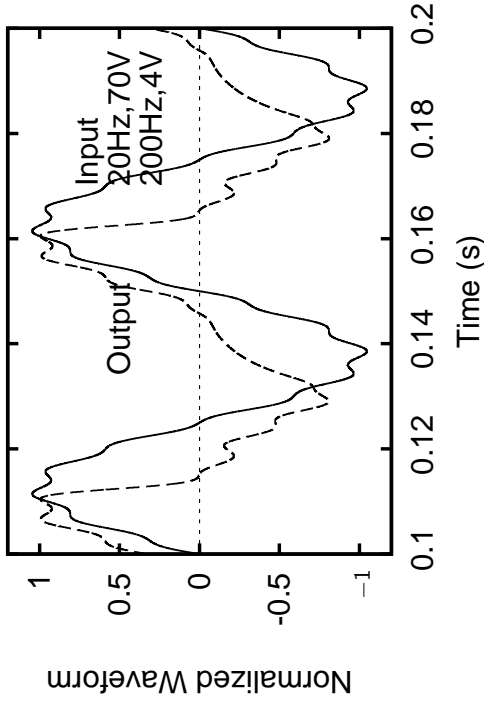
$V_O$  v.s.  $V_I$  with input signal having both low and high frequencies



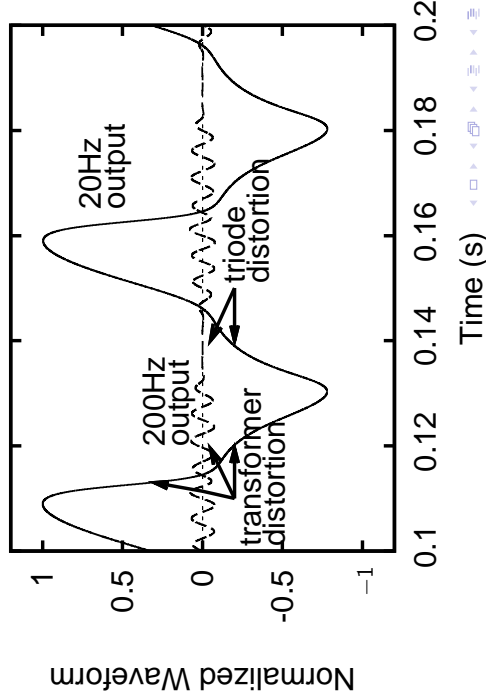Transformer A, low and high frequencies separated for clarity, Speaker Cone Excursion Softly Limited, high frequency not affected by transformer distortion



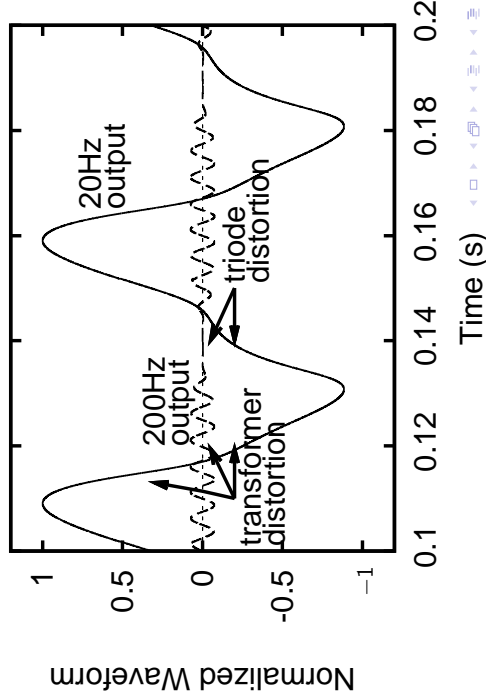
Transformer B, low and high frequencies separated for clarity, Speaker Cone Excursion Softly Limited, high frequency not affected by transformer distortion



Part 2, Tube amplifiers are related to existing speaker cone excursion soft limiters
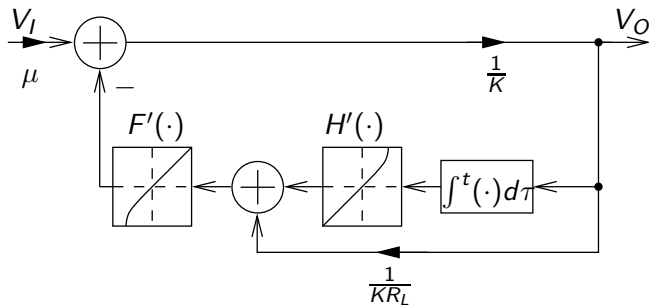
# Simplified block diagram


- ▶ No power filtering (Assume perfect power supply)
- ▶ Non-linear functions approximated with linear and non-linear parts






# Block Diagram Manipulation...

- Reorganize junctions

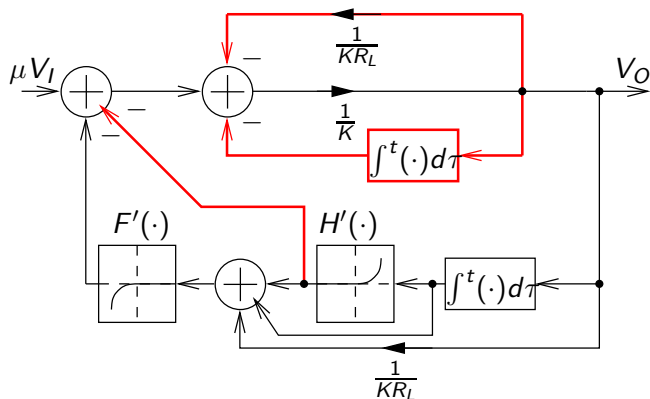

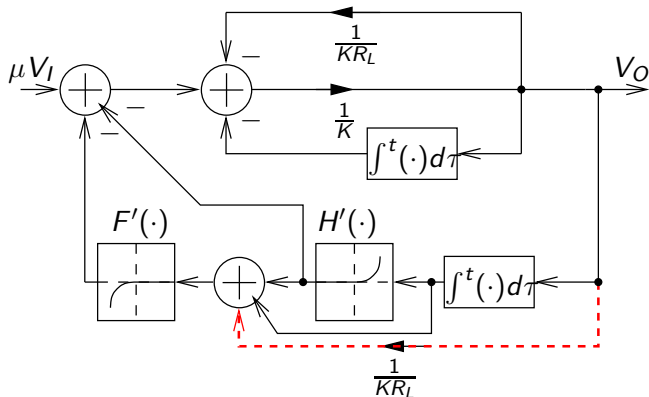
# Block Diagram Manipulation...

- ▶ Further simplified by removing the speaker feedback
- ▶ One example is with interstage transformers



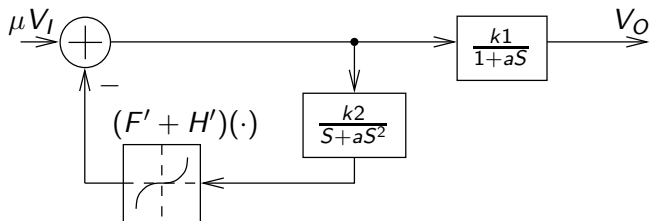
# Block Diagram Manipulation...Done

- ▶ Combine functions
- ▶ How is it compared to the next figure?


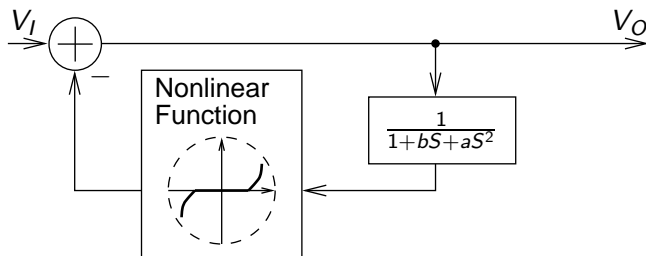
# Klippel's speaker protector

- ▶ This one is typical, other speaker cone excursion limiters exist




## Part 3, Experiments

# Block Diagram Manipulation...Done

- ▶ Compare Simulation with SET (Mostly done)
- ▶ Compare circuit based on block diagrams with SET (Current)
- ▶ Listening test to compare Simulator, SET, and Circuit (Future)

# photos of SET outputs

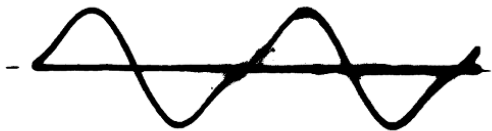

photos of SET outputs

